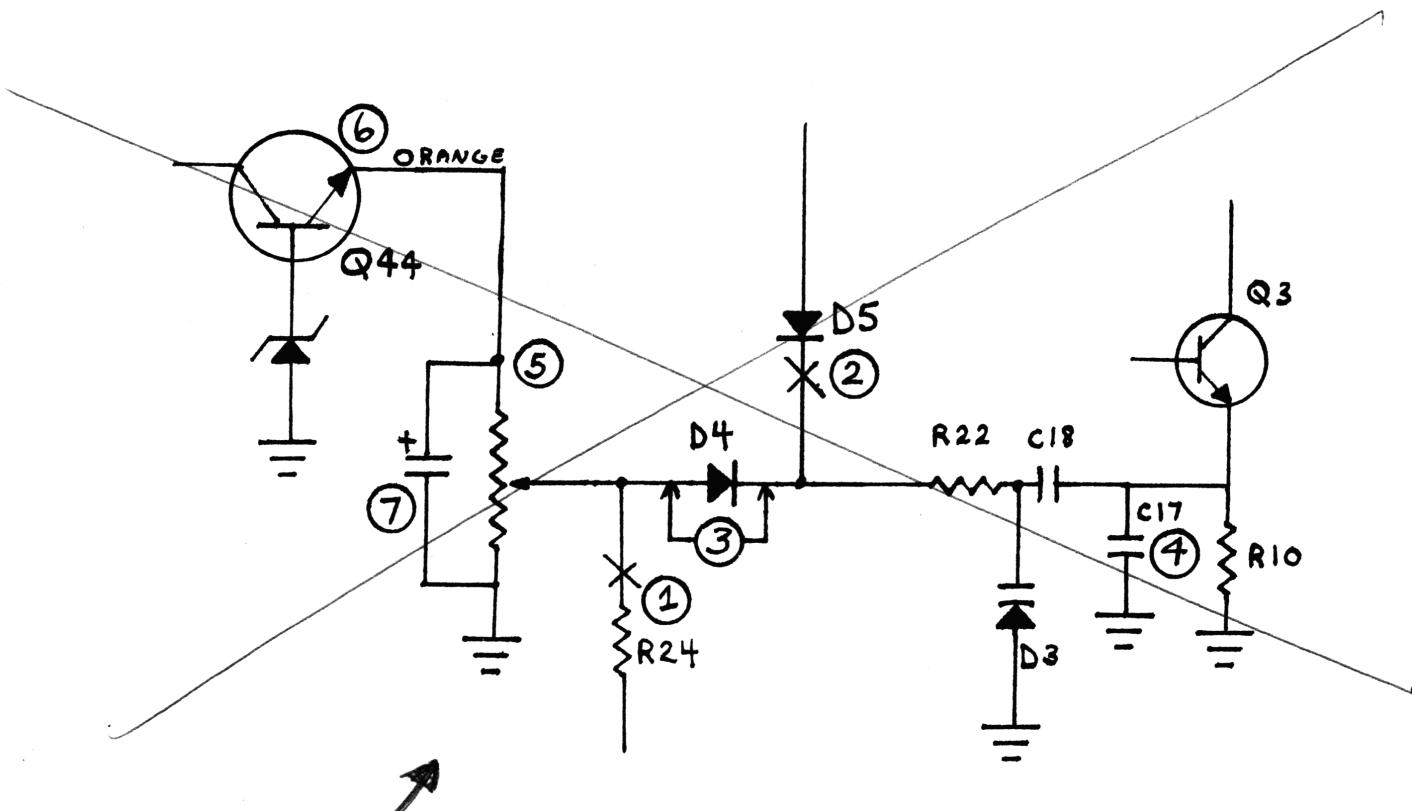


1. Clip R24.
2. Clip D5.
3. Remove D4 and install a solid wire jumper in its place.
4. The value of C17 can be altered slightly for more slide.
5. Solder one end of an Orange wire to the unused end of the Fine Tune control.
6. Solder the other end to the emitter of Q44 voltage Regulator.
7. Add a 47ufd/25V Electrolytic Capacitor on the Fine Tune control. Solder the + lead to the Orange wire (added above) and the - lead to the Black lead.



This SUCKS!! the guy that submitted this probably has a RADIO that is just like it Half ass

1. Sets up nice but when you slide down it drops the transmitter.
2. If you want to make this chassis SLIDE use Vol II pg. 14.